

leads in from the right feeds the current to this group of outlets and can be considered the *source*. The switch at the left controls the outlet next to it, while the pull chain cover has a switch in the base. The outlet at the top is connected to the source in the junction box.

Study Chapters 4 and 5 in "Wiring Simplified" when you do this exercise.

The upper left hand-corner of the panel shows the five steps in making a "Western Union" splice:

1. Twisting the wires
2. Completed splice
3. Soldered
4. Rubber tape
5. Friction tape

This splice is used only for outdoor wiring.

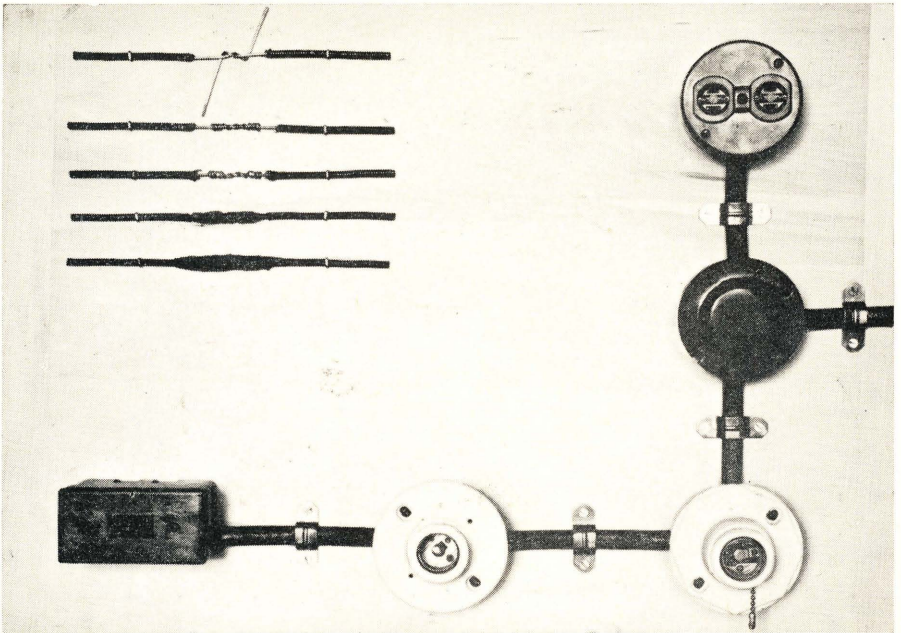


Fig. 26. The completed panel.